

PHILIPS

Design and Implementation of a True Random Number Generator Based on Digital Circuit Artifacts

Michael Epstein, Laszlo Hars, Raymond Krasinski,
Martin Rosner, Hao Zheng
September 9, 2003

Outline

- Description of randomness
- Digital circuit artifacts
 - Meta-stability
 - Jitter
- A practical random number generator
- Prototype measurements
- Conclusion


What is Real Randomness?

- Statistical uniformity
 - Unbiased - 50% of the bits are ones and 50% are zeros
 - Fairness, all sequences are equally likely
- Knowing the past gives no hint of the future
- Derived from physical phenomena
 - Radioactive source
 - Thermal noise
 - Cannot be predicted, because no one has been able to predict it yet!
- Common Problems
 - Complex circuits
 - Physical/circuit size

Premise: Get Randomness from a Digital Circuit


- But the output of any digital circuit is always predictable (when used properly)
 - Digital circuits only manipulate bits
 - Every bit is absolute i.e. it is a one or a zero
 - Given known inputs the output is always the same
 - Ignore pseudo-randomness (that is cheating and all papers on the topic are about when you get caught)
- Suggestion: Do not use the circuit as intended
 - Poor circuit models but **RANDOM BEHAVIOR**

Meta-stability

 


S	R	Q	Qbar	Comment
1	0	1	0	set
0	0	1	0	stable
0	1	0	1	reset
0	0	0	1	stable
1	1	0	0	abnormal
0	0	X	X	meta-stable

Set/Reset Latch

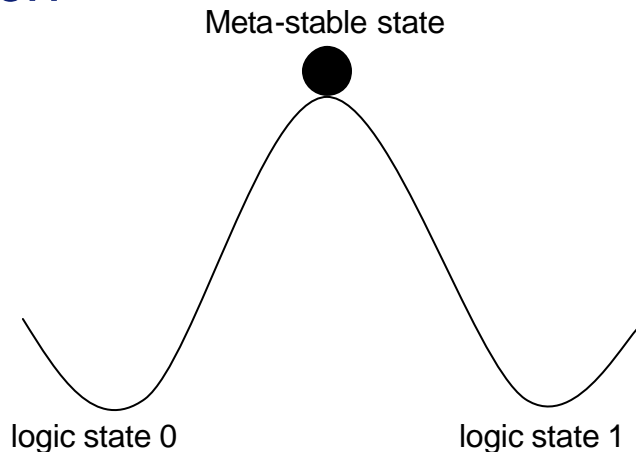


Breadboard Result

 


Flip-flop metastability on Oscilloscope

Previous Work

 


- M.J. Bellido, A.J. Acosta, et al. published in 1992
- Output is biased except under controlled conditions
 - Laser trimmed device
- phenomena was replicated with a relay or mechanical switch

<u>input</u>	<u>Q</u>	<u>Qbar</u>	<u>comment</u>
1	N	N	neutral
0	X	X	meta-stable

 


Jitter

 
- Uncertainty about phase and/or frequency of a repetitive signal
 - Patterned components
 - Random components




The Four Switch Solution

 



Oscillator Mode

 

Resolve mode

 


Silicon Implementation

  

Sources of Randomness

- Ungoverned oscillators have random issues
 - Startup time
 - Low gain is helpful
 - Jitter
 - ❖ Note: Asymmetric delays reject external “locking” attacks
- Bi-stable (resolver) has random issues
 - Meta-stable balance point
 - Meta-stable voltages

 Prototype System, 15 cells, all different



The Piling Up Lemma (handling bias)

- How can we remove bias?
 - The piling up lemma [Matsui 93]; Combination many random outputs biased by b_i produces a random output biased by b
 - b is much smaller than any b_i even if the individual b_i are large and have same kind of bias

$$b = \left| \text{Prob}(X = 1) - \frac{1}{2} \right| = \left| \text{Prob}(X = 0) - \frac{1}{2} \right|$$

$$b = 2^{n-1} \prod_{i=1}^n b_i$$

Testing

- Use the 16 DieHard tests
 - Each test produces a “squeezed” normal result
 - A Pvalue in a range from 0 to 1.000000
 - Very unlikely to find values near the tails (near 0 or 1)
- Rate each Pvalue as
 - A “hard”, “near” failure or “good”
 - Allow very few hard failures and/or a small number of near failures
 - Retest marginal cases if needed
 - Sometimes a random result will appear non-random but not on a consistent basis

Results



- Tested several designs
 - For each design we tested 15-31 varieties and XOR of all varieties
 - Each design was replicated 8 times
- The best design (4-switch)
 - Is random for some varieties
 - At some voltages
 - Is random for XOR of 15 varieties over voltage range of 1.2 – 2.0 volts (1.8 is nominal)

Detailed Results


- No special layout or custom circuits were used
 - Some identical cells passed and or failed
 - Suggests small layout changes have an affect
 - Each (XOR) copy requires 164 gates (very practical!!)
- At any voltage almost all of the varieties fail but the XOR always passes for all 8 copies
 - The results are random but biased
 - De-biasing always yields bits that pass

Thanks

  - Martin Rosner
 - circuit design
 - breadboard implementation
- Laszlo Hars, Hao Zheng
 - random theory
 - circuit design
- Raymond Krasinski
 - software support
- Philips Semiconductors


 
```
Main(argv,argc)
{
    goto void;
}
```



Conclusions

- Practical real random number generator can be built from standard digital circuits
 - Stable over voltage variations
- Work remains
 - Show good randomness over temperature change
 - Combination of voltage and temperature change
 - Verify physical source of randomness
 - Hopefully in the quantum mechanical sense
 - Verify resistance to electrical attacks

